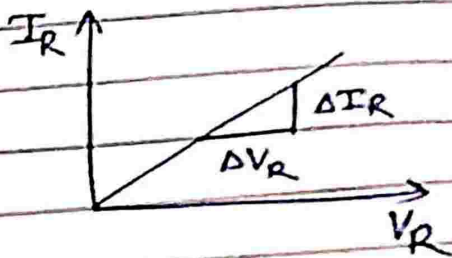


## Ohm's law

Ohm's law states that the voltage across a linear element is directly proportional to the current flowing through it.


$$V \propto I$$

$$V = IR \quad (\text{for resistive circuit})$$



$$R = \frac{\Delta V_R}{\Delta I_R}$$

Resistor  $\rightarrow$  linear.

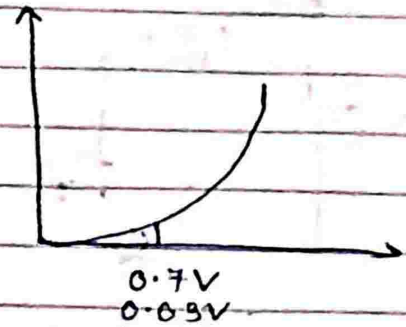

diode  $\rightarrow$  non linear

$$V_C = \frac{1}{C} \int I_C(t) dt$$

$$V_L = -L \frac{dI_L(t)}{dt}$$

Capacitor  
Inductor

## Kirchhoff's law :-

- 1) KCL  $\rightarrow$  K - Current Law
- 2) KVL  $\rightarrow$  K - Voltage Law

### KCL




KCL states that the algebraic sum of all the currents getting into the junction is zero.

$$\sum_{j=1}^n I_j = 0$$

### KVL


The algebraic sum of all the voltage drops around the closed loop is zero.

$$\sum_{j=1}^n V_j = 0$$

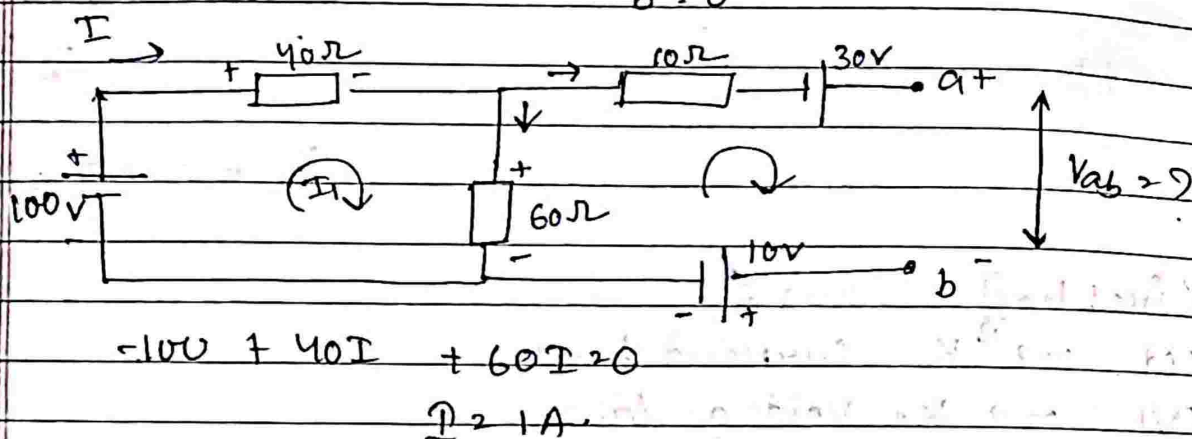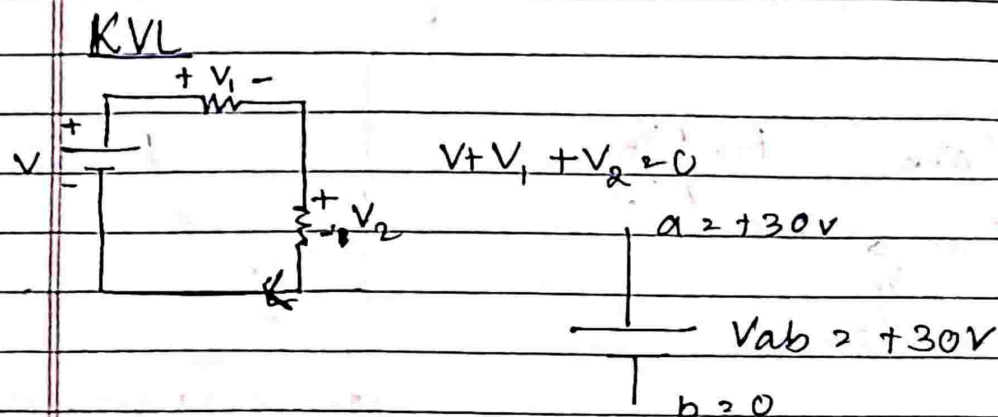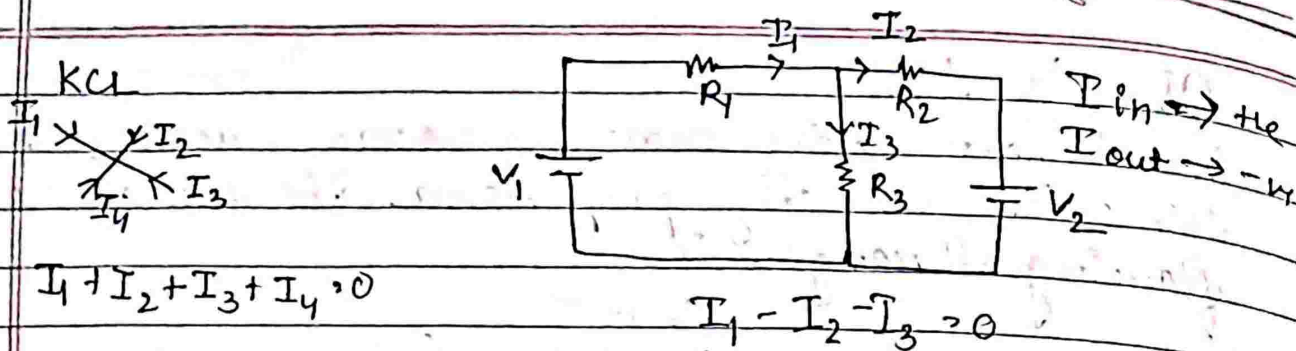


$10 - 60 - 30 + V_{ab} = 0$  | no current; voltage drop = 0 in  $10\Omega$  resistor

$V_{ab} = 80$

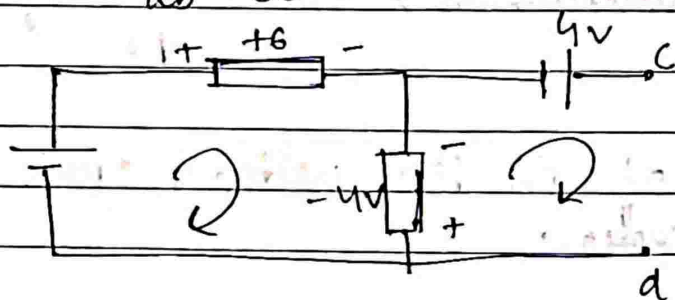

$-6V + 4V + V_{cd} = 0$   
 $V_c = +2V$

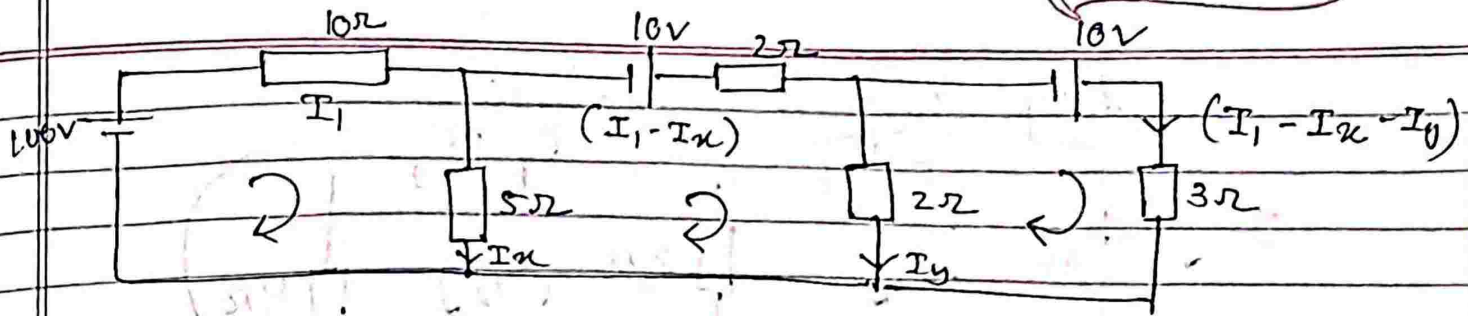

$$-100 + 10I_1 + 5I_x = 0$$

$$2I_1 + I_x = 20$$

$$-10 + 2(I_1 - I_x) - 2I_y - 5I_x = 0$$

$$-10 + 2I_1 - 2I_x - 2I_y - 5I_x = 0$$

$$2I_1 + 7I_x + 2I_y = 10$$

$$-10 + 3(I_1 - I_x + I_y) + 2I_y = 0$$

$$3I_1 - 3I_x + 3I_y + 2I_y = 10$$


$$3I_1 - 3I_x + 5I_y = 10$$

using matrix rule,

$$\begin{bmatrix} 10 & 5 & 0 \\ -2 & 7 & 2 \\ 3 & -3 & 5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_x \\ I_y \end{bmatrix} = \begin{bmatrix} 100 \\ -10 \\ 10 \end{bmatrix}$$



## Loop Current Analysis

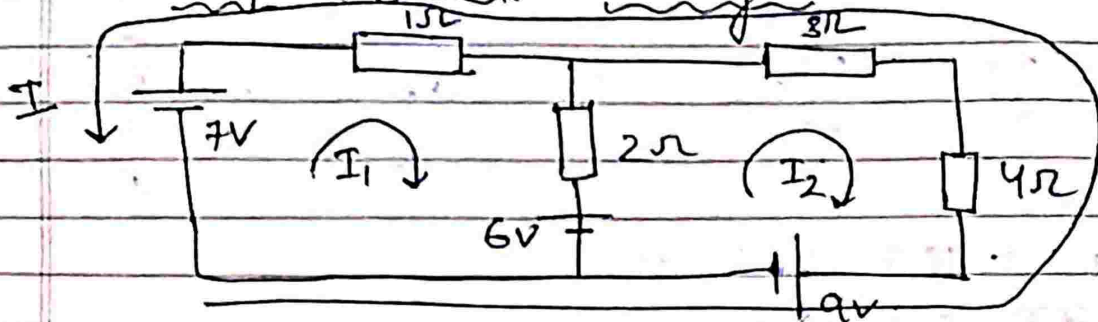

$\sum \text{Voltage drop across resistors} = \sum (+ \text{ or } -) \text{ Voltage sources in the loop}$

$$1I_1 + 2(I_1 - I_2) = +7 - 6 \Rightarrow 3I_1 - 2I_2 = 1$$

$$(I_2 - I_1)2 + I_2 3 + I_2 4 = -9 + 6 \Rightarrow 3I_1 = 1 + 2I_2$$

$$2I_2 - 2I_1 + 7I_2 = -3 \Rightarrow I_1 = \frac{1 + 2I_2}{3}$$

$$9I_2 - 2I_1 = -3$$

$$9I_2 - 2\left(\frac{1 + 2I_2}{3}\right) = -3$$

$$9I_2 - \frac{2}{3} - \frac{4I_2}{3} = -3$$


$$\frac{23}{3}I_2 = -\frac{7}{3}$$

$$I_2 = -7/23 \approx -0.304$$

$$I_1 = \frac{1 - 14/23}{3} = \frac{9/23}{3} = \frac{3}{23} \approx 0.13$$


Outer loop (consider I and I<sub>1</sub>)

$$7I + 1(I - I_1) = -7 + 9$$

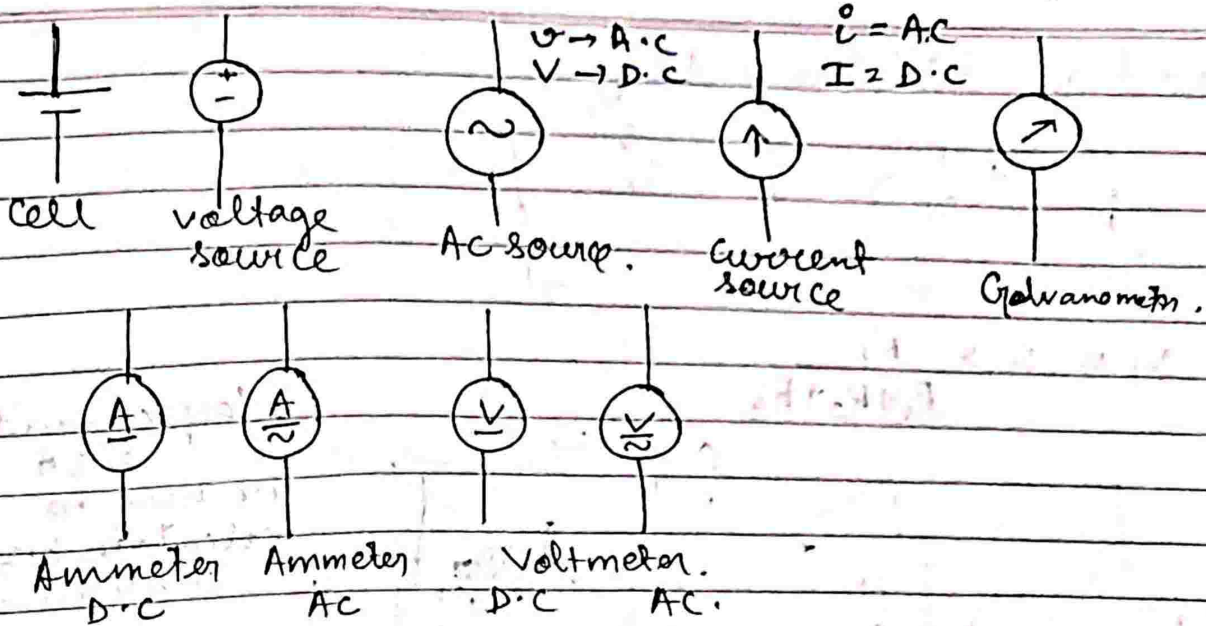


Voltage source in series.  
Current source in parallel.

## Source Transformation

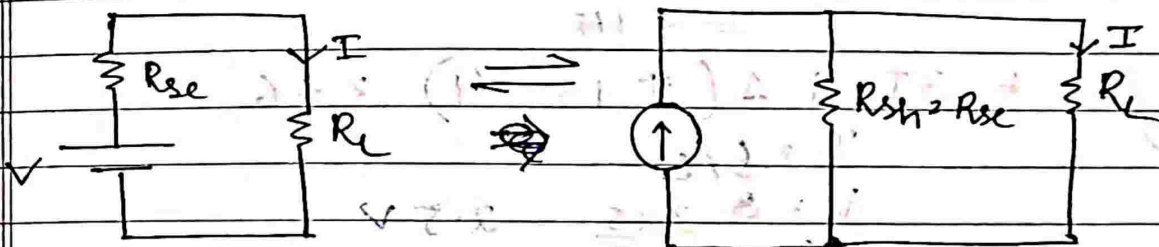

$$\frac{V}{R_{se}} = I$$


## Current Division Rule

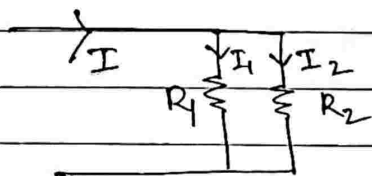


$$I_1 = \frac{R_2}{R_1 + R_2} \times I$$

$$I_2 = \frac{R_1}{R_1 + R_2} \times I$$

Voltage division rule:

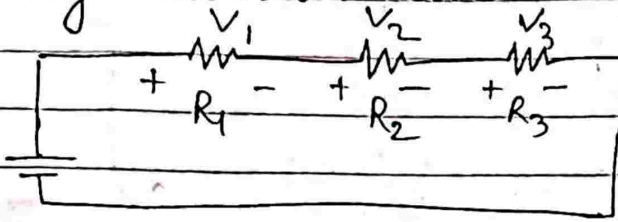
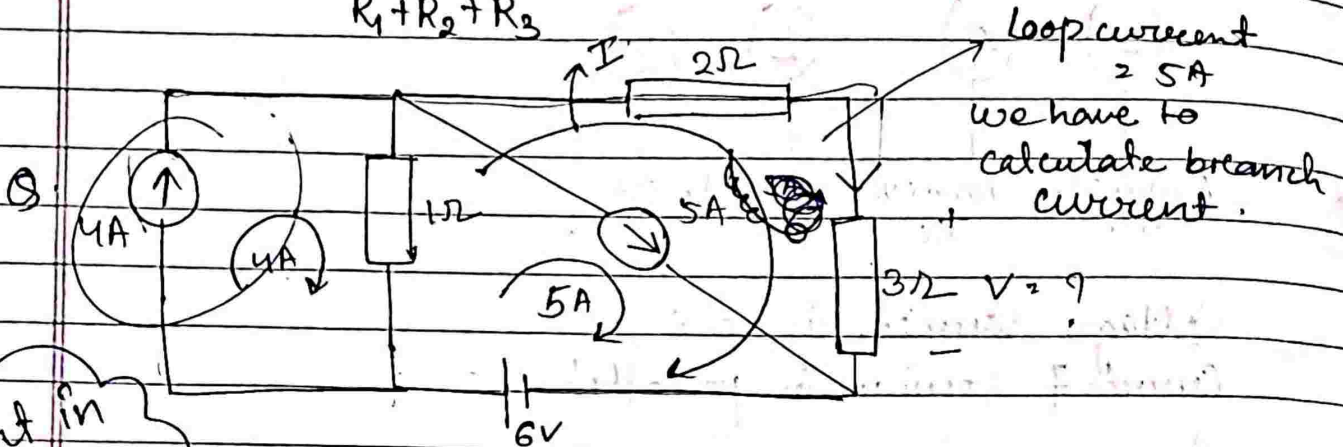
$$V_1 = V \times \frac{R_1}{R_1 + R_2 + R_3}$$



Current in any 1 loop can be 5 A are total in both loop can be 5A

$$2I + 3I + 1I = 6$$

$$I = 1A$$

$$2I + 3I + 1(I + 5 - 4) = 6$$

$$I = 5/6$$

$$V = 3 \times \frac{5}{6} = 2.5V$$

$$I = \frac{V}{R}$$

$$I = \frac{V}{R}$$





## Dependent and Independent loop

An independent loop is a loop, the current of which doesn't depend on the current of any other loop.


To identify the independent loop, one has to replace the sources in the electrical circuit with their equivalent resistance.

Voltage source with closed circuit.

Current source with open circuit.

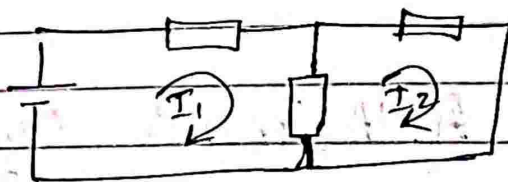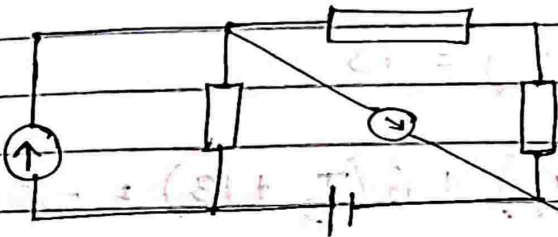

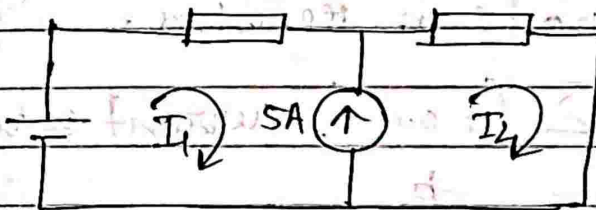
$I_1$  &  $I_2$  are independent  
→ independent loop.



$$|I_1 - I_2| = SA$$

→ dependent loop.

## Mesh Analysis

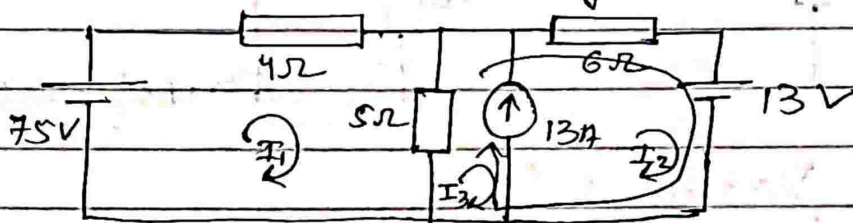

A mesh is the smallest loop in a electrical circuit.  
A mesh can <sup>also</sup> be considered as a loop, but a loop may not always be a mesh.

To handel current source, the concept of super mesh has been developed.

If the current source is common to two different meshes then both mesh can be combined to form a super mesh.

Mesh 1 :-  $4I_1 + 5(I_1 - I_3) = 75$

Super mesh  $5(I_3 - I_1) + 6(I_3 + 13) = -13$

Pre-define step

$I_2 - I_3 = 13$


Always consider current leaves from a node.

## NODE VOLTAGE ANALYSIS

use when current source is given

$\sum \text{current leaving the node in resistor} = \sum (+ \text{ or } -) \text{ current entering the node}$

Node a

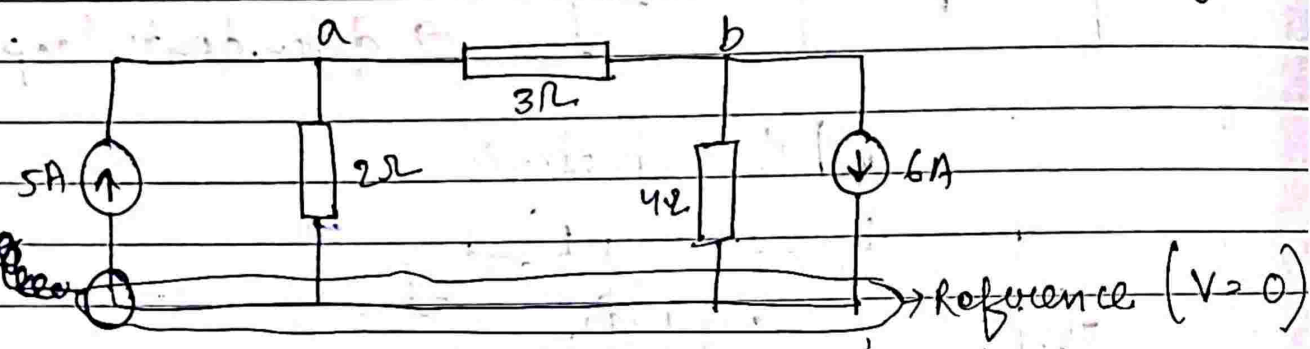

Node a

$\frac{V_a - 0}{2} + \frac{V_a - V_b}{3} = 5$

Node b

$\frac{V_b - 0}{4} + \frac{V_b - V_a}{3} = -6$



$$5 - \frac{V_a}{2} = 6 + \frac{V_b}{4}$$

$$\frac{V_b}{4} + \frac{V_b - 2V_b + 2}{3} = -6$$

$$-\frac{V_b}{4} - \frac{V_a}{2} = 6 - 5$$

$$\frac{3V_b - 4V_b + 8}{12} = -6$$

$$-\left(\frac{2V_b - V_a}{2}\right) = 1$$

$$8 - V_b = -12 \times 6$$

$$V_a - 2V_b = -2$$

$$V_b = 72 + 8 = 80$$


$$V_a = 2V_b - 2$$

$$V_a = 160 - 2 = 158$$

$$V_a = 2V_b - 2 = 0 \text{ or } V_a = 2V_b - 2$$

$$V_a = 9.5 \text{ V}$$

$$V_b = -8.88 \text{ V}$$

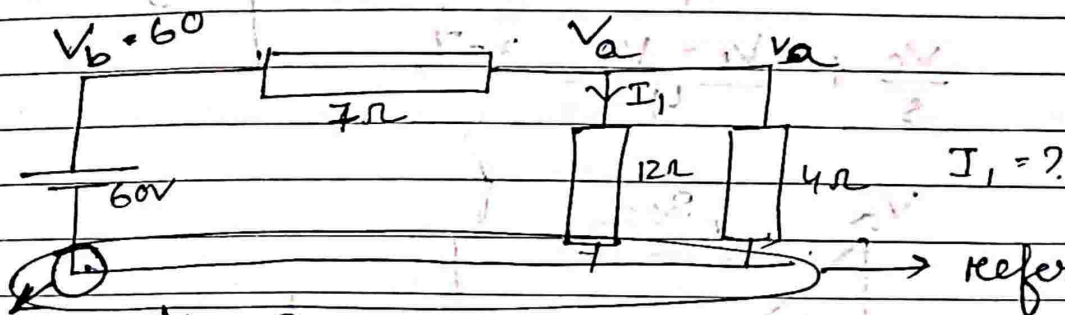

Non floating voltage source connected to the reference node source


$$\frac{V_a - 0}{12} + \frac{V_a - 60}{7} = I_1$$

$$7V_a + 12V_a - 12 \times 60 = I_1 \times 84$$

$$\frac{V_a}{12} + \frac{V_a}{7} - \frac{V_a - 60}{7} = 0$$

floating node

super node.  $V_b - V_a = -6$

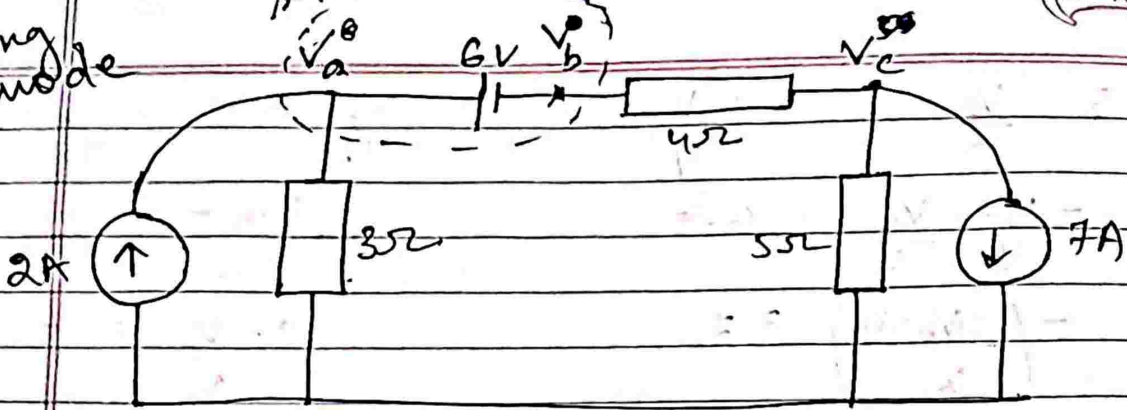

$V_a$   
 $V_b$   
 $V_c$  } = ?


~~$V_a + V_b + V_c = 20$~~   
 ~~$V_a + V_b - V_c = 2$~~   
 ~~$V_c + V_c - V_b = 7$~~

$$\frac{V_a}{3} + \frac{V_b - V_c}{4} = 2$$

$$\frac{V_c}{5} + \frac{V_c - V_b}{4} = 7$$

$$\begin{aligned} V_a &= -2.75 \\ V_b &= -8.77 \\ V_c &= -20.43 \end{aligned}$$

Q.

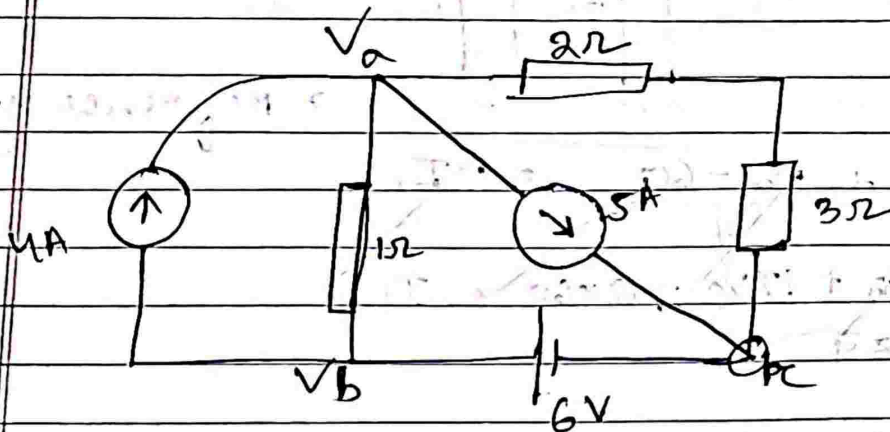

$$\frac{V_a - 6}{1} + \frac{V_a}{5} = 4 - 5$$

$$V_a = 4.17 \text{ V}$$

$$\frac{4.17 \times 3}{5} = 2.4 \text{ A}$$




# Network Theorems

## Superposition Theorem.

The response in a linear circuit at any point due to multiple sources can be calculated by summing the effects of each source considered separately, or <sup>all</sup> other sources being made inoperative (open circuit for current source, short circuit for voltage source.)


~~Dependent Source~~

## Dependent Source

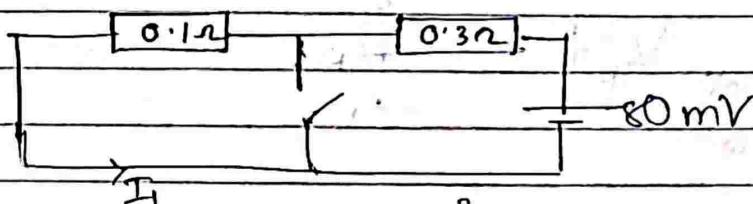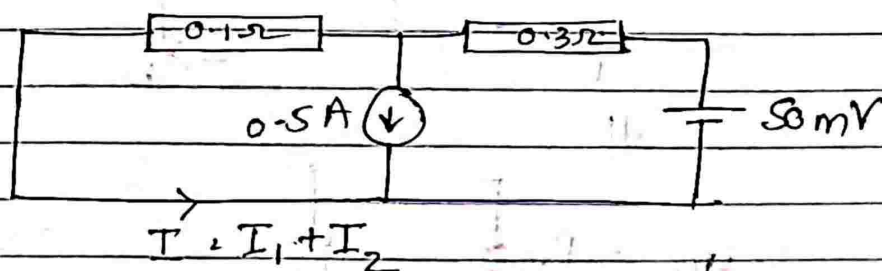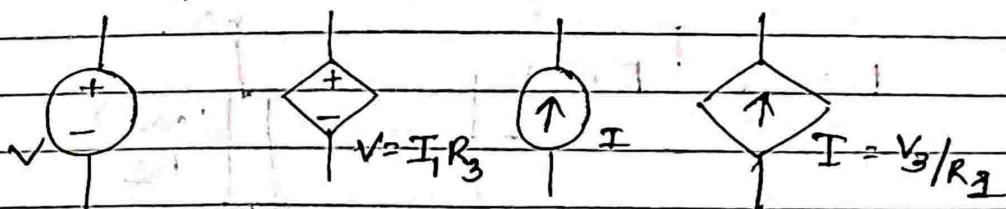

$$I_1 = \frac{80 \times 10^{-3}}{0.4}$$

$$= 0.2A$$

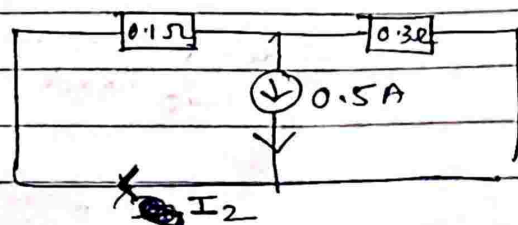

$$I_2 = \frac{0.5 \times 0.3}{0.4}$$


$$= \frac{1.5}{4} = 0.37$$

$$I = 0.2 - 0.37 = -0.17$$




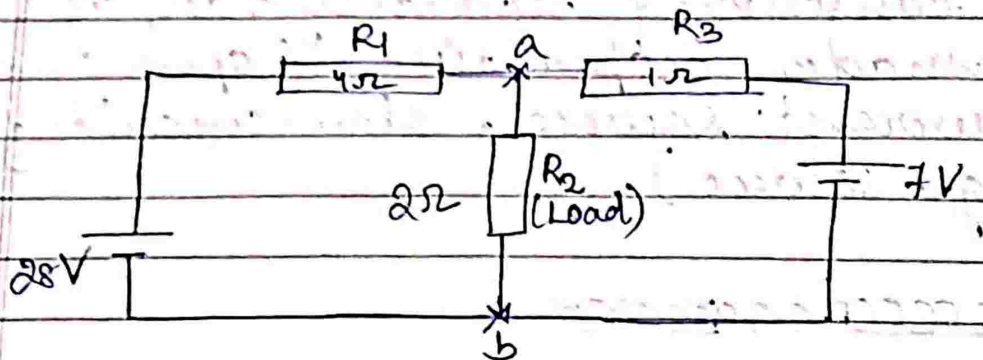
## Thevenin's Theorem

Thevenin's Theorem states that it is possible to simplify any linear circuit containing independent & dependent source, to an equivalent circuit with a voltage source ( $V_{Th}$ ) in series with a resistance ( $R_{Th}$ ) between any 2 terminals in the circuit.



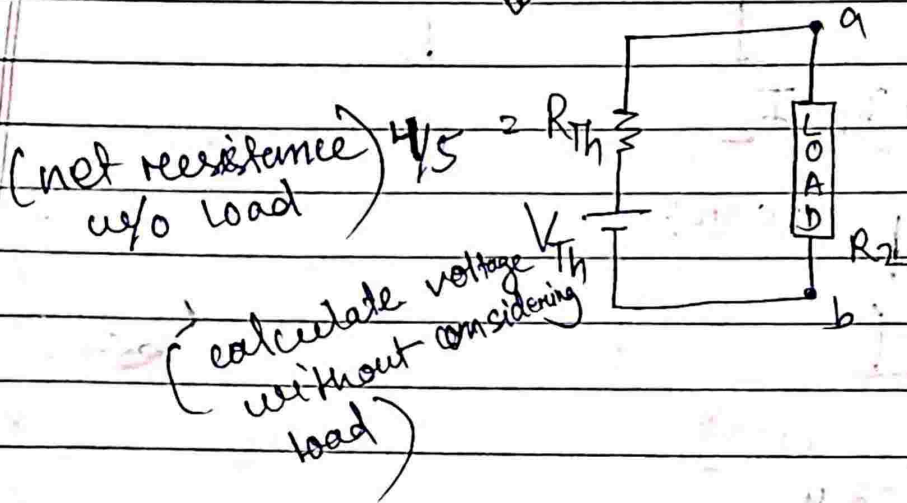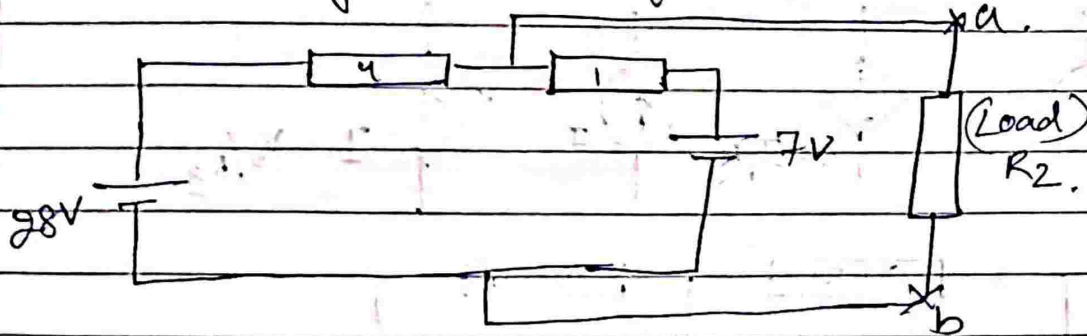
# Circuit obeys the law of superposition - linear circuit



(net resistance w/o load)  $4/5 = R_{Th}$

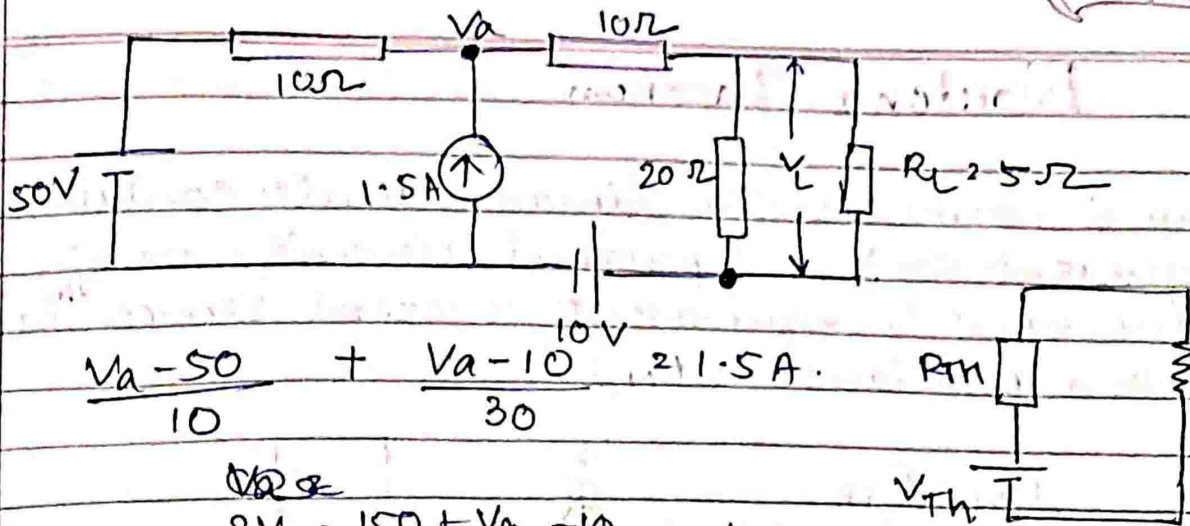(calculate voltage  $V_{Th}$  without considering load)



$$\frac{V_a - 50}{10} + \frac{V_a - 10}{30} = 1.5 \text{ A}$$

~~1.5A~~

$$\frac{3V_a - 150 + V_a - 10}{30} = 1.5$$

$$4V_a - 160 = 45$$

$$4V_a = 205$$

$$V_{\text{across } 20\Omega} = V \times \frac{20}{30}$$

$$= \frac{2(51.25 - 10) \times 2}{3}$$

$$= \frac{41.25 \times 2}{3} = 27.5$$



$$V_{TH} = 27.5$$

## Norton's Theorem

Any 2 terminal of a linear circuit containing dependent and independent circuit can be converted to equivalent current source  $(I_N)$  in parallel with a resistance  $(R_N)$

$$R_N = R_{Th}$$

$$I_N = \frac{V_{Th}}{R_{Th}}$$

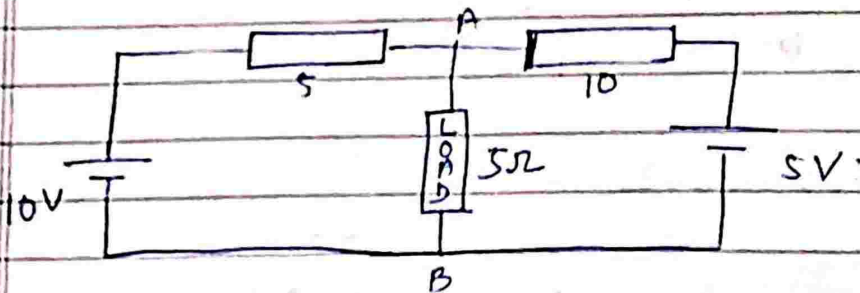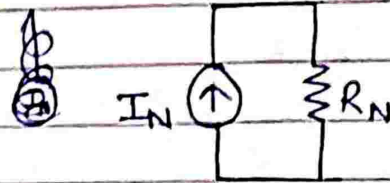

$$R_N = \frac{10 \times 5}{10 + 5}$$

$$R_N = \frac{10 \times 5}{15} = \frac{10}{3}$$

$$I_N = \frac{18}{2 \times \frac{10}{3} + 2} = \frac{18}{\frac{20}{3} + 2} = \frac{18}{\frac{26}{3}} = \frac{18 \times 3}{26} = \frac{54}{26} = 2.5$$




## Maximum Power Transfer

Maximum power is absorbed from a network when the load resistance is equal to the output resistance of the network as seen from the load side

$$P = I^2 R_L$$
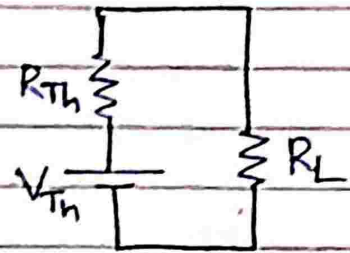
$$P = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$




$$\frac{dP}{dR_L} = 0$$

$$R_{Th} = R_L$$

Impedance Matching

## Star-Delta Transformation

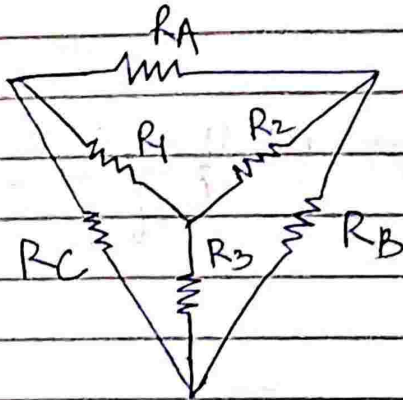

$\Delta \rightarrow Y$

$$R_1 = \frac{R_A R_C}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$Y \rightarrow \Delta$

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$